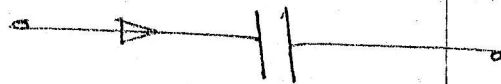


Exam 2007

a current varies with time as shown in fig  
 sketch the variation of the voltage produced by this current  
 flowing in an initially uncharged capacitor  $C = 10^{-6} \text{ f}$


11



$+$   $V(t)$   $-$

$$V(0) = 0$$

$$i(t) = C \frac{dV(t)}{dt}$$

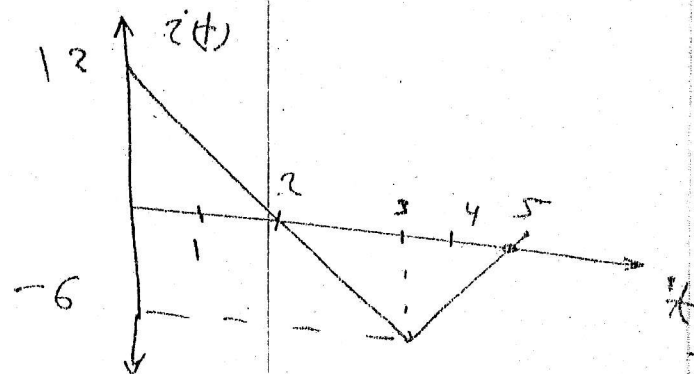

$$V(t) = \frac{1}{C} \int i(t) dt$$

$$= \frac{1}{10^{-6}} \int i(t) dt = 10^6 \int i(t) dt$$

$$V(t) = \begin{cases} 0 & t < 0 \\ -\frac{18}{2}t + 12 & 0 \leq t \leq 3 \\ \frac{6}{2}t + A & 3 \leq t \leq 5 \\ 0 & t > 5 \end{cases}$$

$$V(3) = -18 + 12 = -6$$

$$\therefore -6 = \frac{6}{2} \times 3 + A \rightarrow A = -15$$

$$V(t) = \begin{cases} 0 & t < 0 \\ -3t^2 + 12t + B & 0 \leq t \leq 3 \\ \frac{3}{2}t^2 - 15t + C & 3 \leq t \leq 5 \\ D & t \geq 5 \end{cases}$$

$$v(0) = \text{Zur}$$

12

$$\therefore 0 = 0 + 0 + B \rightarrow B = 0$$


$$v(3) = -27 + 36 + 0 \rightarrow v(3) = 9$$

$$\therefore 9 = \frac{3}{2}(3)^2 - 15 \times 3 + C \rightarrow C = 40.5$$

$$v(5) = \frac{3}{2}(5)^2 - 15 \times 5 + 40.5 = 3$$

$$\therefore D = 3$$
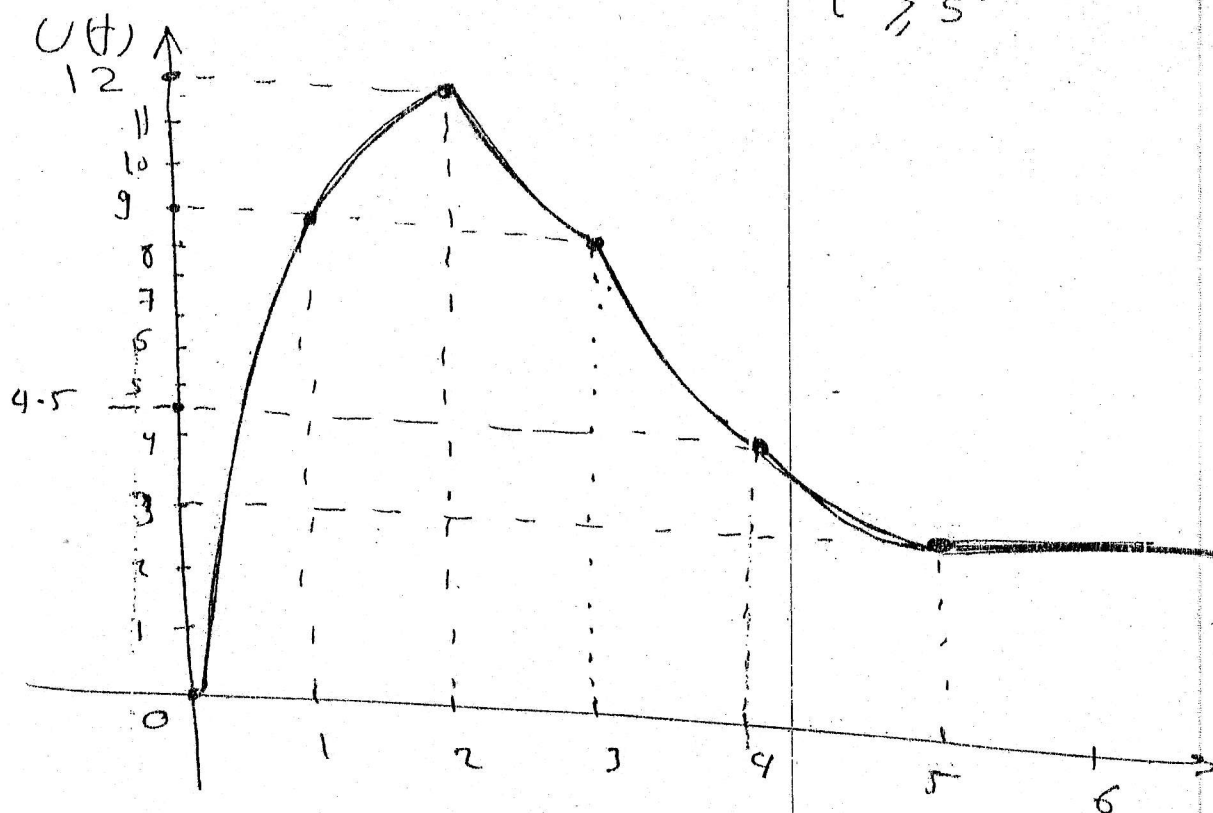
$$v(t) = \begin{cases} 0 & t < 0 \\ -3t^2 + 12t + 0 & 0 \leq t \leq 3 \\ \frac{3}{2}t^2 - 15t + 40.5 & 3 \leq t \leq 5 \\ 3 & t \geq 5 \end{cases}$$



16] The energy stored in a  $0.02 \text{ f}$  Capacitor with  $440 \text{ volts}$  across it is transferred to a  $1.2 \text{ H}$  inductor what is the current in the inductor

حفظ  $W_C = \frac{1}{2} C V^2$

$C = 0.02$

$V = 440$

$W_C = W_L$

find  $i$

$W_L = \frac{1}{2} L i^2$

$L = 1.2 \text{ H}$


$\therefore \frac{1}{2} C V^2 = \frac{1}{2} L i^2$

$0.02 \times (440)^2 = 1.2 \times i^2$


$\therefore i = \sqrt{\frac{0.02 \times (440)^2}{1.2}}$

$\approx 56.8 \text{ A}$

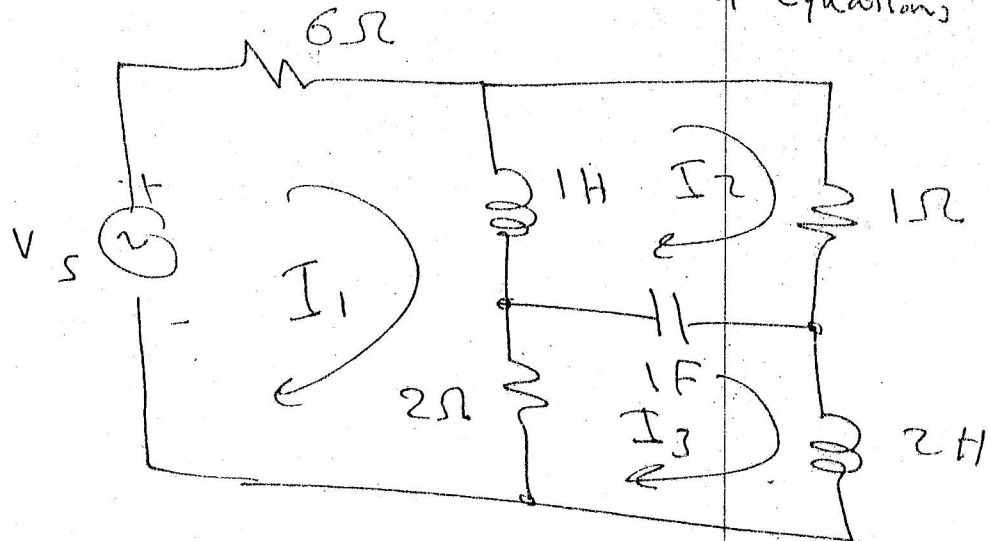
17] Draw the graph of the circuit, Tree, write Loop equations



Graph

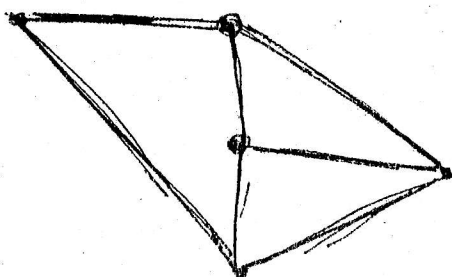

Tree

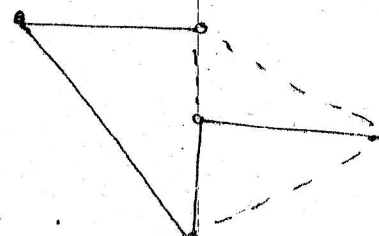

$N = 4$

K.V.L for Loop 1

$$V_s = 6 I_1 + 1 \frac{d(I_1 - I_2)}{dt} + 2 (I_1 - I_3)$$


K.V.L for Loop 2

$$0 = \frac{d(I_2 - I_1)}{dt} + \frac{1}{1} \int (I_2 - I_3) + 1 I_2$$

K.V.L for Loop 3

$$0 = 2 (I_3 - I_1) + 1 \int (I_3 - I_2) + 2 \frac{d I_3}{dt}$$

3

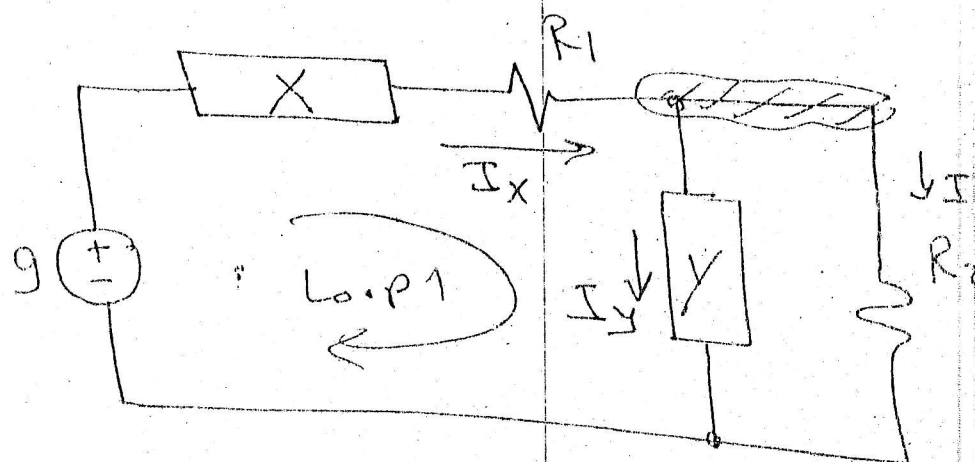

if

$$V_x = 4 \text{ Volts}$$

$$I_x = 1.5 \text{ mA}$$

$$V_y = 2 \text{ V}$$

$$I_y = 1 \text{ mA}$$


Find  $R_1, R_2$

Solution

$$I_x = 1.5 \text{ mA} = I_{R_1}$$

$$I_y = 1 \text{ mA}$$
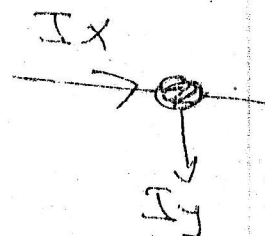
$$\therefore I = I_x - I_y = 1.5 \text{ mA} - 1 \text{ mA} = 0.5 \text{ mA}$$



$$V_y = V_{R_2}$$

$$\therefore R_2 = \frac{V_y}{I} = \frac{2}{0.5 \text{ mA}} = 4 \text{ k}\Omega.$$

K.V.L for Loop 1

$$+9 + V_x + \underbrace{I_x R_1}_{V_{R_1}} + V_y = 0$$


$$\therefore V_{R_1} = 9 - V_x - V_y$$

$$= 9 - 4 - 2 = 3 \text{ V}$$

$$\therefore R_1 = \frac{3}{1.5 \text{ mA}} = 2 \text{ k}\Omega.$$

4 If the switch is closed to a at  $t=0$  and is transferred to b at  $t=5 \text{ sec}$  sketch the variation of the current  $i$  with time for  $0 < t < 10 \text{ sec}$ .


14

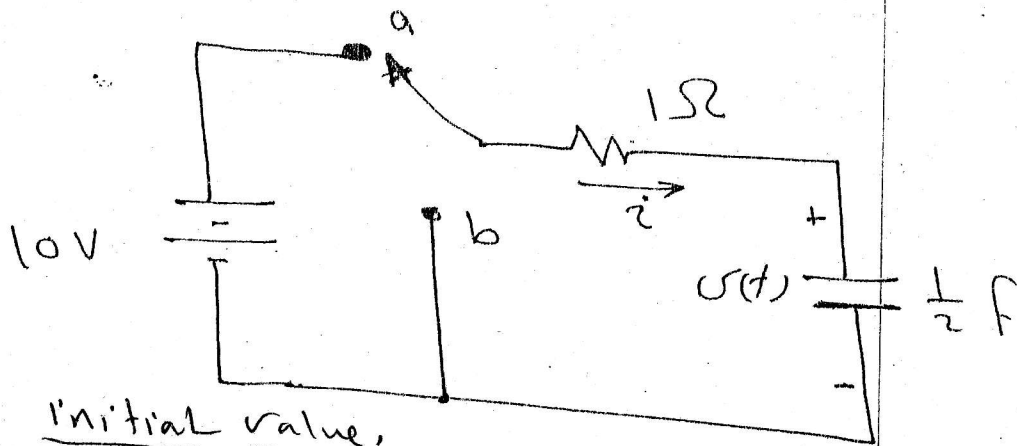

Initial value:  
if,  $t < 5 \text{ sec}$

$$i(5) = 0$$

$$u(5) = 10 \text{ V}$$

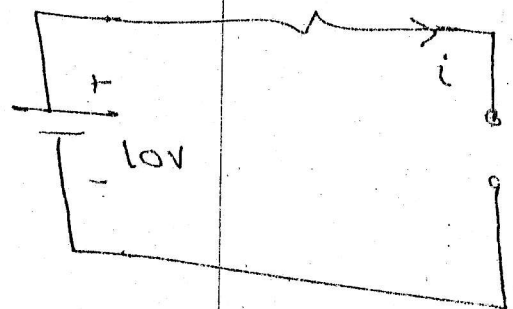

if  $t \geq 5 \text{ sec}$

$$0 = \frac{du(t)}{dt} \left( \frac{1}{2} \right) + \frac{u(t)}{R}$$

$$0 = \frac{du(t)}{dt} + 2 u(t)$$


$$u_c(t) = k e^{-2(t-5)}$$

$$u_p(t) = 0$$


$$\therefore u(t) = k e^{-2(t-5)}$$

$$u(5) = 10 = k \rightarrow k = 10$$

$$\therefore u(t) = 10 e^{-2(t-5)}$$

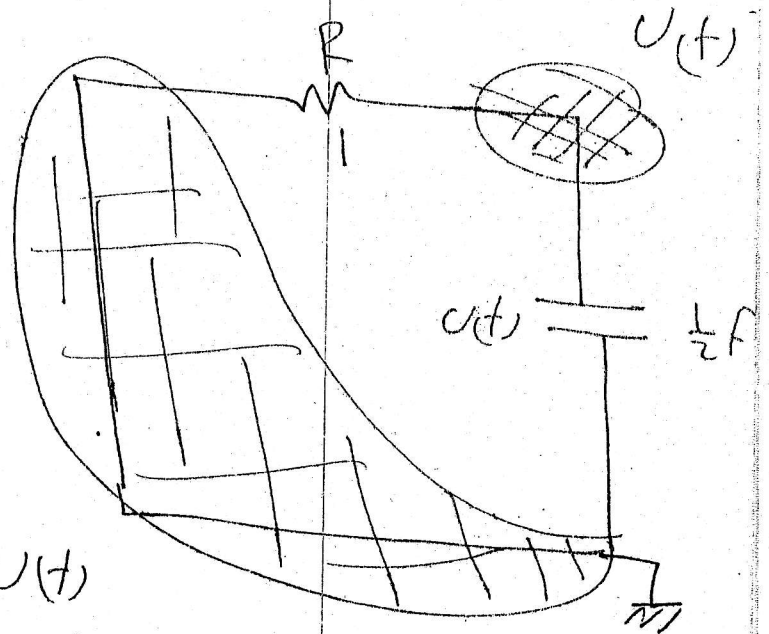

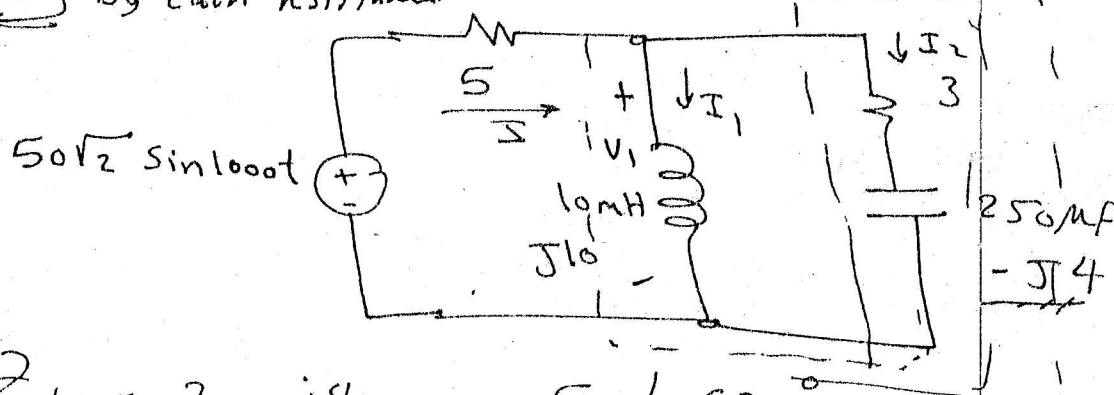5 Find the power output from the source, power absorbed by each resistance.



$$Z_1 = 3 - j4 = 5 \angle -53.13^\circ$$

$$Z_2 = \frac{j10 \times 5 \angle -53.13^\circ}{j10 + 3 - j4} = \frac{10 \angle 90^\circ \times 5 \angle -53.13^\circ}{3 + j7} = \frac{50 \angle -36.87^\circ}{7.61 \angle 66.8^\circ}$$

$$Z_T = 5 + 6.57 \angle -30^\circ = 5 + 5.68 - j3.2 = 10.689 - j3.2 = 11.15 \angle -16.6^\circ$$

$$\therefore I = \frac{50 \angle 0^\circ}{11.15 \angle -16.6^\circ} = 4.48 \angle 16.6^\circ$$

$$I_1 = 4.48 \angle 16.6^\circ \times \frac{6.57 \angle -30^\circ}{3 + j10 - j4} = \frac{29.46 \angle -13.4^\circ}{6.7 \angle 63.4^\circ} = 4.39 \angle -76.8^\circ$$

$$V_1 = I_1 \times X_L$$

$$\therefore V_1 = 4.39 \angle -76.8^\circ \times 10 \angle 90^\circ$$

$$= 43.9 \angle 13.2^\circ$$

$$S_1 = I_1^* V_1$$


$$= 4.39 \angle 76.8^\circ \times 43.9 \angle 13.2^\circ$$

$$= 192.7 \angle 89.9^\circ$$

$$S_1 = 0 + j192.7 = 192.7 \angle 90^\circ$$

$$P_R = |I|^2 \times R$$
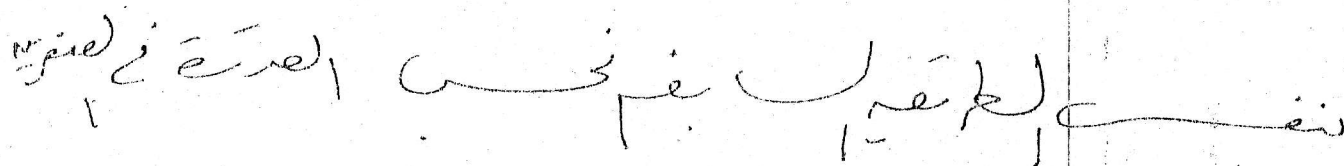
$$= (4.98)^2 \times 5 = 100.35 \text{ watt}$$




$$R = 3\Omega$$



متروله وفاعله  
للطالب

Find  $i(t)$

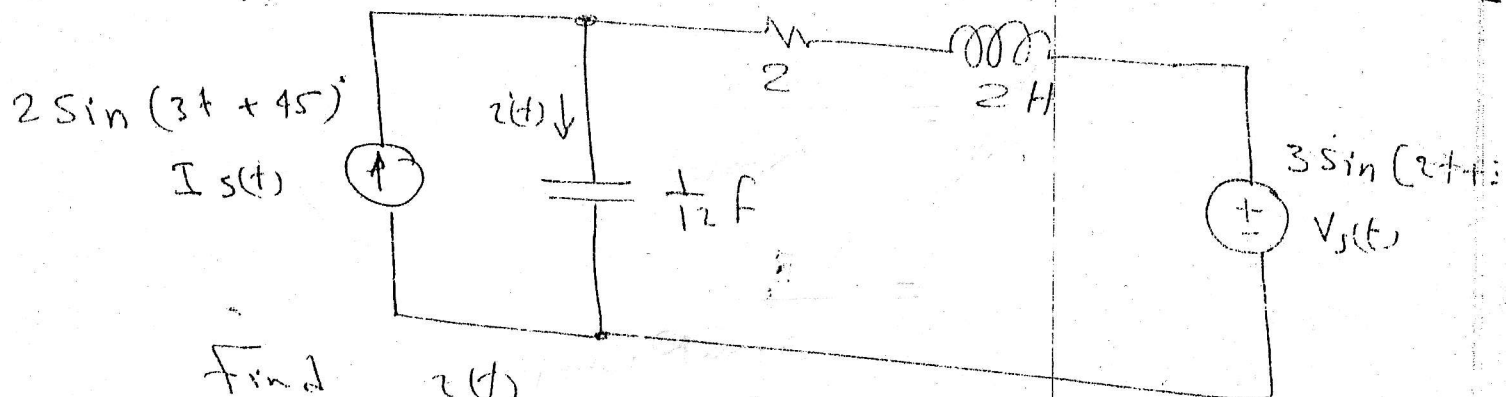


Find  $i(t)$


Solution

Using Superposition:

$$i(t) = i_1'(t) + i_2'(t)$$

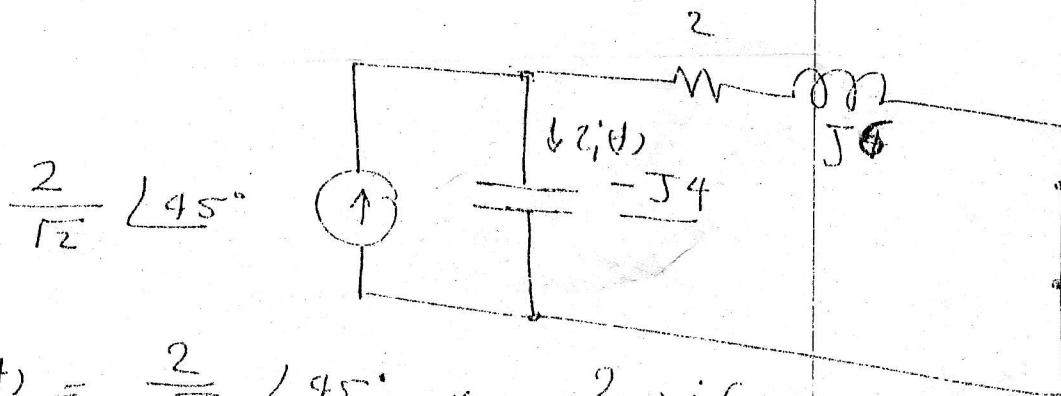
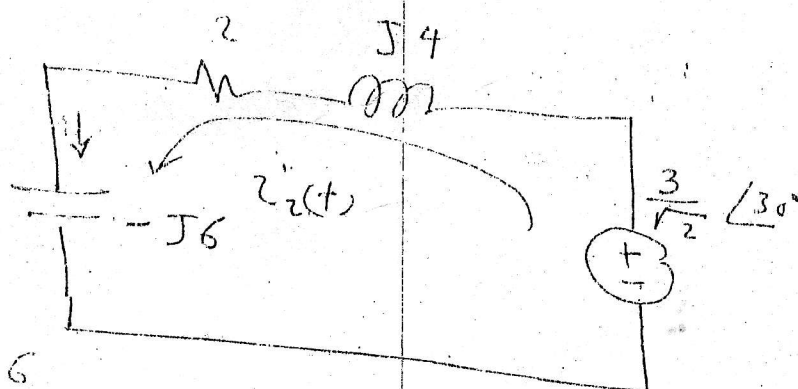
$$i_1'(t) = \frac{2}{r_2} \angle 45^\circ \times \frac{2 + j6}{2 + j6 - j9}$$



$$i_2'(t) = \frac{\frac{3}{r_2} \angle 30^\circ}{2 + j4 - j6}$$

$$i(t) = i_1'(t) + i_2'(t)$$

متروله واهله

للطالب

بالحول

متر و لے

للطالب